

**ADVD**  
**Assignment 2**  
**EEE F313**

Problem set 14



Sai Kartik (2020A3PS0435P)  
Rajeev Rajagopal (2020A3PS1237P)  
Manpreet Singh (2020A3PS0419P)

Contents

1 Problem statement 1

2 Design 2

2.1 Circuit diagram . . . . . 2

2.2 W/L calculations . . . . . 2

2.2.1 W/L table . . . . . 2

3 Plots and results 3

3.1 Bode plot for AC gain and phase . . . . . 3

3.2 ICMR plot . . . . . 3

3.3 Slew rate . . . . . 4

3.4 Differential output voltage swing . . . . . 5

3.5 Power consumption . . . . . 5

3.6 Input and output offset voltage . . . . . 5

3.6.1 Input offset voltage . . . . . 5

3.6.2 Output offset voltage . . . . . 6

4 Design Challenges 6

List of Figures

1 Circuit diagram . . . . . 2

2 AC gain at . . . . . 3

3 ICMR plot . . . . . 3

4 Slew rate . . . . . 4

5 Differential output voltage swing . . . . . 5


6 Output offset voltage . . . . . 6

List of Tables

1 Table for W/L values . . . . . 2
 
## 1 Problem statement

Design a two stage CMOS OPAMP as shown in the figure



- (a) Analysis of all equations of your design, with a systematic derivation of all transistors W/L ratios and spectre simulation of circuit for the following specifications:
  - (i) Open loop gain (DC gain)  $\geq 110\text{dB}$
  - (ii) Phase margin  $\approx 60^\circ$
  - (iii) Power dissipation  $\leq 1\text{mW}$
- (b) Show a biasing circuitry to bias all the voltages in your design (except the input)
- (c) Calculate and plot the following parameters for your OPAMP: DC gain, Bode plot for AC gain and phase, ICMR plot, slew rate, Differential Output voltage swing (dc+transient), power consumption, and input and output offset voltage.

## 2 Design

### 2.1 Circuit diagram

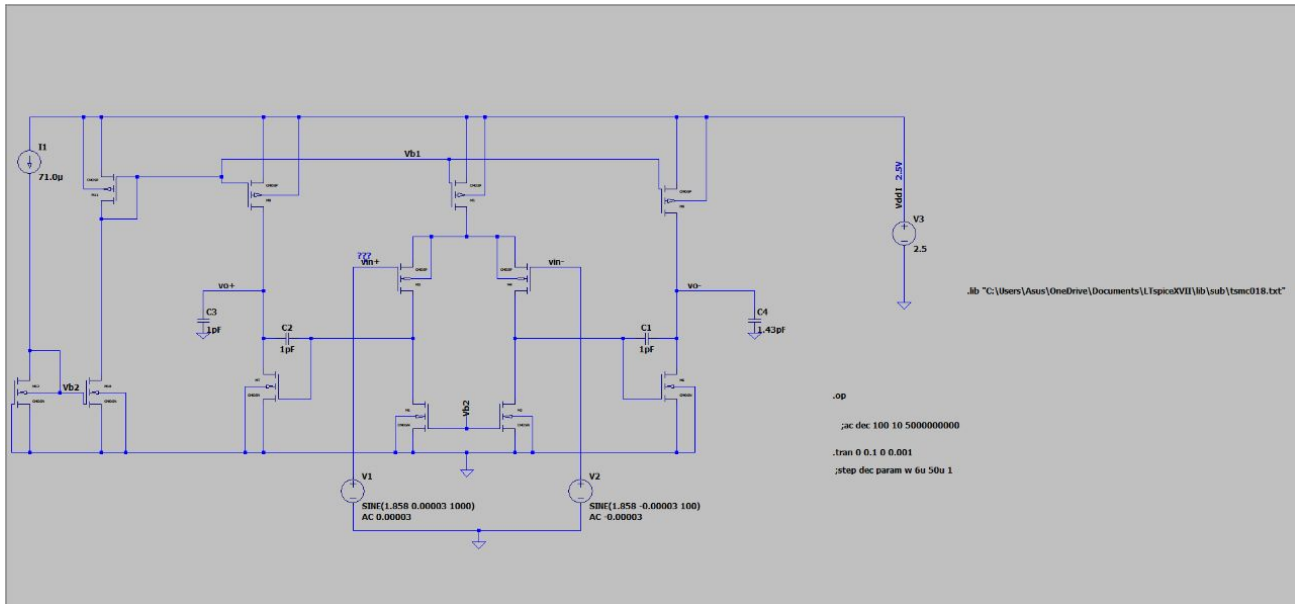


Figure 1: Circuit diagram

### 2.2 W/L calculations

- Current will be same in all the branches of the circuit. Approximate value of  $|V_{DS}|$  was calculated accordingly.
- PMOS overdrive was set at 0.36V and NMOS overdrive at 0.3V because of the lesser mobility of PMOS, which hence needs a higher overdrive voltage.
- To obtain W/L of all the MOSFETs:
  - The MOSFETs were taken to a separate SPICE file.
  - Since the L value is constant, the value for W was found by parametrically sweeping accordingly to match requirements

#### 2.2.1 W/L table

MOSFET	W	W/L
M1 & M2	5.6 $\mu$	16
M3 & M4	5.6 $\mu$	99
M5	65.8 $\mu$	188
M6 & M7 & M10 & M12	2.8 $\mu$	8
M8 & M9	56 $\mu$	160
M11	16.55 $\mu$	47

Table 1: Table for W/L values

### 3 Plots and results

#### 3.1 Bode plot for AC gain and phase



Figure 2: AC gain at

UGB from the given circuit is 218.776 MHz.

With the current circuitry and number of stages the maximum gain we are able to achieve is 66.48dB at 27 °C. The gain can be increased by adding more stages at the expense of power consumption.

#### 3.2 ICMR plot

 


Figure 3: ICMR plot

### 3.3 Slew rate

 


Figure 4: Slew rate

### 3.4 Differential output voltage swing



Figure 5: Differential output voltage swing

### 3.5 Power consumption

Power consumed by the circuit is given by the product: Total current drawn  $\times V_{dd}$   
From the circuit simulated by LTSpice, we have the total current drawn as  $I_{tot} = 329.4\mu A$  and  $V_{dd} = 2.5V$ .  
Hence the total power consumption:  $I_{tot} \times V_{dd} = 329.24\mu A \times 2.5V = 0.8321mW \leq 1mW$

### 3.6 Input and output offset voltage

The input is an AC voltage of  $30\mu$  sinusoid with a frequency of 1kHz. The DC offset voltage given is 1.858V.

#### 3.6.1 Input offset voltage

The input offset voltage is negligible due to the circuit being systematic at the input nodes

### 3.6.2 Output offset voltage

Output offset voltage( $V_{oo}$ ) is defined as follows: Output voltage of the op-amp when both inputs are 0.  $V_{oo}$  is due to dissimilarities in the transistors and due to mismatch in resistor values in the internal circuitry in the op-amp. For this particular calculation, input was set as 0 and transient analysis was performed, which gives us the graph below for small time periods. For larger time periods, a steep fall was observed

The output offset voltage is determined to be 38.089 mV.

 


Figure 6: Output offset voltage

## 4 Design Challenges

1. It was very tedious to match the W/L values from both hand calculations and SPICE simulations. Trial and error was used to eventually reach an optimal value of W/L for each transistor.
2. Obtaining parameters for a 2-stage op-amp was very tricky because of various factors like intermediate poles and separate biasing voltages of all stages
3. No option of a pole and zero plot is available in LTSpice. Individual bode plots had to be used.